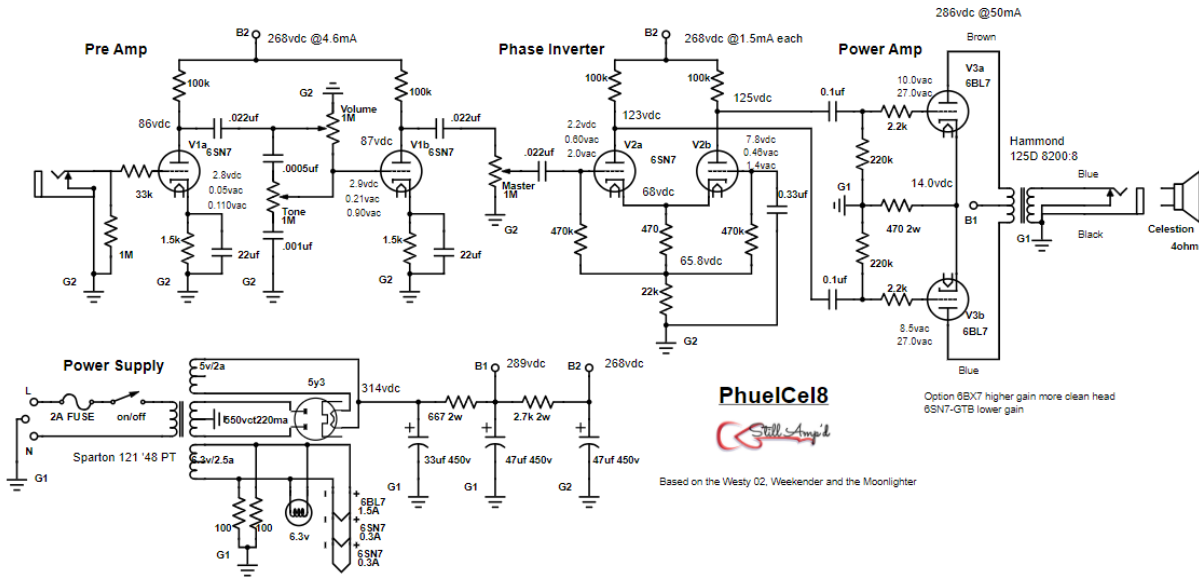


PhuelCel8



PreAmp Design

Pre Amp Case 1

$R_a = 270v/9ma = 30k \text{ ohm}$ (red line)

With original $100k \text{ I}_{plate} = 3ma$ (blue line)

$R_{bias} = 3v/2ma = 1.5k$

Bias center = $-5v$; $V=155v$; $I=4.1ma$

$R_b = 5/4.1ma = 1.22k \text{ ohms}$

Bias = $-6v$, $V=160$, $I=3.7ma$

$R_b = 6/3.7ma = 1.62k \text{ ohms}$

Bias = $-7v$; $V=175$, $I=3ma$

$R_b = 7/3ma = 2.33k \text{ ohms}$

Pre Amp Change:

Change R_a from $100k$ to $30k \text{ ohm}$ $V= 155vdc$ (green dot); 55% of supply


Leave R_b at $1.5kohms$; bias $\sim 5.7v/3.8ma$

Stage Two

Same design as Preamp

Pre Amp

6SN7GT

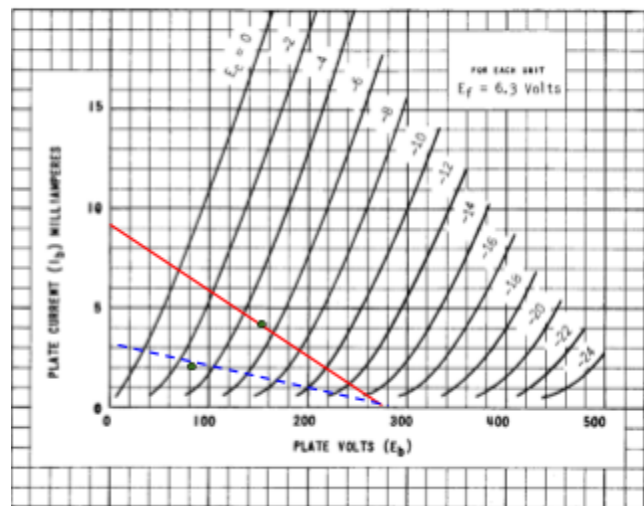

PhuelCel8

Phase Inverter

Case 1

$$B2 = 270v$$

$$V_{tail} = 70v \text{ (26\% of } B2)$$

$$V_{triode} = 200v$$

$$I_{triode} = 6.5ma$$

$$R_{plate} = 200v/6.5ma = 30.8kohm$$

Bias

$$V_{bias} = -6v$$

$$I_{bias} = 2ma$$

$$R_{bias} = 6v/(2*2ma) = 1.5kohm$$

Tail

$$R_{tail} = (70v-6v)/(2*2ma) = 16kohms$$

Conclusion:


Change R_a from 100k to 30k ohm $V = 160vdc$

Change R_b from 470 to 1500ohms

Change R_{tail} from 22k to 16kohm

Phase Inverter

6SN7GT

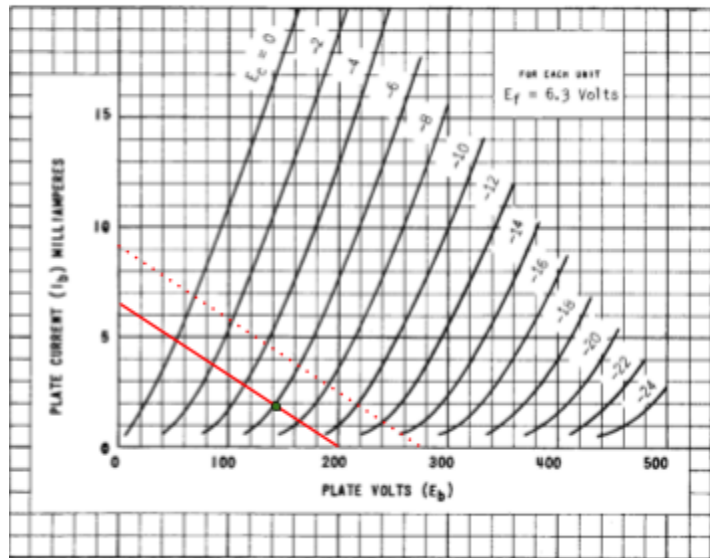

Phase Inverter Case 2

$$B2 = 290v; 9ma \text{ 6SN7 typical spec}$$

$$V_{tail} = 70v \text{ (24\% of } B2)$$

$$V_{triode} = 220v$$

$$I_{triode} = 7.5ma$$

$$R_{plate} = 220v/7.5ma = 29.3kohm$$

Bias

$$V_{bias} = -6v$$

$$I_{bias} = 2.5ma$$

$$R_{bias} = 6v/(2*2.5ma) = 1.2kohm$$

Tail

$$R_{tail} = (70v-6v)/(2*2.5ma) = 12.8kohms$$

Phase Inverter Conclusion:


Change R_a from 100k to 30k ohm $V = 150vdc$ (green dot); 68% of supply (150/220)

Change R_b from 470 to 1.2kohms; $V_{bias} = -6v$

Change R_{tail} from 22k to 12.8kohm; $V_{tail} = 64v$

Phase Inverter

6SN7GT

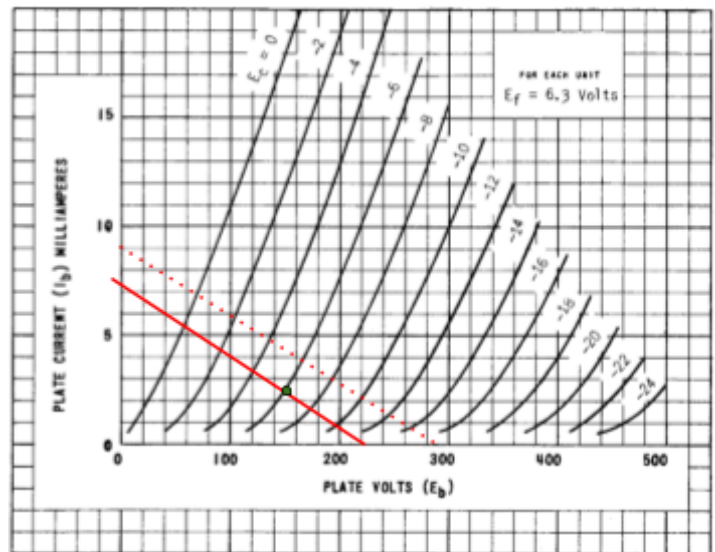

PhuelCel8

Power Stage

Case 1 - 8.2kohm (125D 2&5)

B1 = 290vdc

$$I_{classA} = 290v / (8200 / 2) = 70.7ma$$

$$I_{classB} = 290v / (8200 / 4) = 141.5ma$$

$$\text{Bias} = -14v; R_{bias} = 14v / 15ma = 933ohm$$

$$\text{Power} = 260v * 15ma = 3.9w$$


$$\text{Bias} = -5v; R_{bias} = 5v / 45ma = 111ohm$$

$$\text{Power} = 200v * 45ma = 9w$$

$$14 - x / 14 - 5 = 933 - 470 / 933 - 111$$

$$14 - x = 9 * 463 / 822$$

$$x = 14 - 9 * 463 / 822 = 8.9v$$

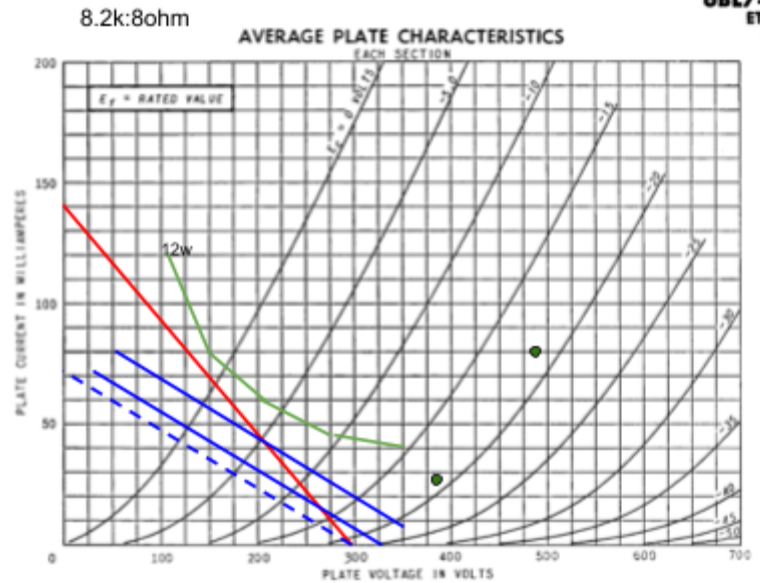

Case 2 - 11.6kohm (125D 1&4)

B1 = 290vdc

$$I_{classA} = 290v / (11600 / 2) = 55.8ma$$

$$I_{classB} = 290v / (11600 / 4) = 100ma$$

$$\text{Bias} = -5v; R_{bias} = 5v / 35ma = 142ohms$$


$$\text{Power} = 285v * 35ma = 10w$$

$$\text{Bias} = -10v; R_{bias} = 10v / 20ma = 500ohms$$

$$\text{Power} = 182v * 35ma = 6.4w$$

$$\text{Bias} = -14v; R_{bias} = 14v / 12ma = 1166ohms$$

$$\text{Power} = 282v * 12ma = 3.4w$$

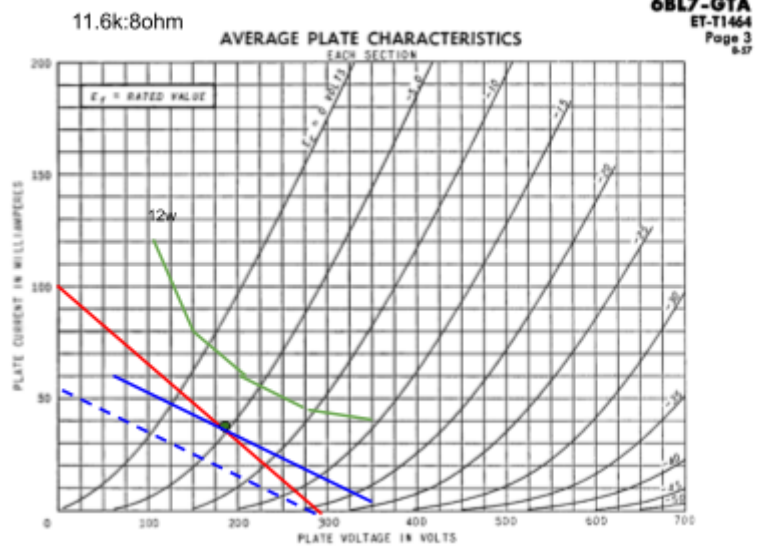

PhuelCel8

Power Stage Case 3 -

$R_{ot} = 11.6\text{k}\Omega$ (125D 1&4)

$B1 = 315\text{Vdc}$

$I_{classA} = 315\text{V}/(11600/2) = 54.3\text{mA}$

$I_{classB} = 315\text{V}/(11600/4) = 108.6\text{mA}$

Bias = -5V ; $R_{bias} = 5/40\text{mA} = 125\Omega$

Power = $200\text{V} \cdot 40\text{mA} = 8\text{W}$

Bias = -10V ; $R_{bias} = 10/25\text{mA} = 400\Omega$

Power = $240\text{V} \cdot 25\text{mA} = 6\text{W}$

Bias = -15V ; $R_{bias} = 15/12\text{mA} = 1250\Omega$

Power = $275\text{V} \cdot 12\text{mA} = 3.3\text{W}$

Power Stage Conclusion -

apply B1a 315V to plate

Use 1&4 from 125D for 11.6k:8ohm

Keep R_{bias} at 470ohms for $V_{bias} = -10.4\text{V}$;

