

Fig. 5-11: Conventional Power Amp Master Volume


paraphase drive signals are at whatever level the input stage determines to be appropriate to make the feedback signal look like the input signal. If we attenuate these paraphase signals, the input stage must work harder to obtain the required feedback. At some point, the input stage runs out of gain and output capability and begins to distort. The output signal is then distorted as well. The greatest distortion occurs when the interstage level controls are set low. Less signal is transferred from the input stage to the output stage.

It would seem that the intent of the master volume is to produce distortion. Indeed, this is generally true, and the power amplifier master volume does not allow a truly clean sound to be set up, as the conventional master volume is able to do. This means that the power amp master is restricted to those situations where the amp is being set up for one range of tones only—distorted ones.

### Typical Power Amp Master Volume Installations

There are two popular methods for installing power amp master volumes. The first is the preferred method, as it is safer and easier to implement. Fig. 5-12A illustrates an AC-coupled master volume pot.  $C_1$  and  $C_2$  are the

### A PREFERRED

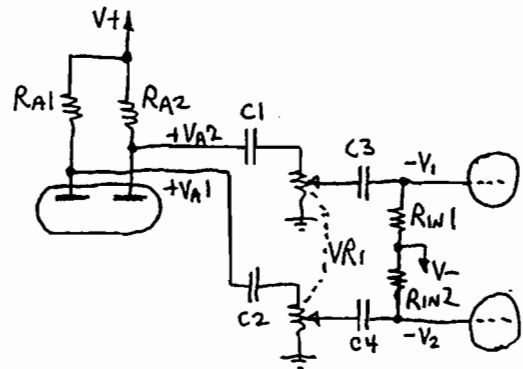

### B NOT RECOMMENDED

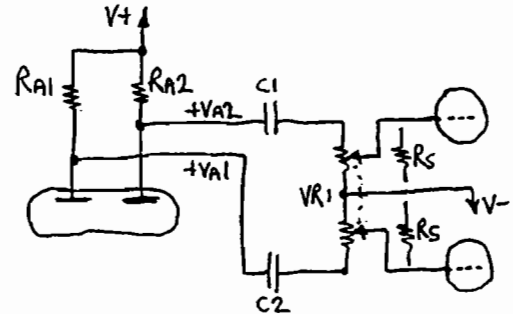


Fig. 5-12: Typical Power Amp Master Volumes

original coupling caps from  $R_A$  to  $R_{IN}$ . These block the high positive voltages present on the anodes of the input stage, from  $VR_1$ .

To block the negative bias voltage on the grids of the output tubes from the master volume control, we must add  $C_3$  and  $C_4$ . These caps are effectively in series with  $C_1$  and  $C_2$ , and could have a negative influence on the low-frequency response of the amp. Capacitors in series behave as:

$$C_{TOTAL} = \frac{C_1 \times C_2}{C_1 + C_2}$$

$C_{TOTAL}$  can never be larger than the smaller of the two capacitance values. So, to avoid excess change in the low-frequency response, the new

## PREAMP MODIFICATIONS

caps should be at least ten times the value of the original caps. Where  $C_1$  and  $C_2$  must have a voltage rating suitable to block  $V+$ ,  $C_3$  and  $C_4$  must only block  $V-$ .  $C_3$  and  $C_4$  could have 100V ratings to provide an ample safety margin, while still allowing the use of plastic caps.

In Fig. 5-12B, we see a way to eliminate  $C_3$  and  $C_4$ . Several allegedly knowledgeable people have suggested this method, but it is VERY DANGEROUS, and we do not recommend it! The method involves replacing the bias feed resistors ( $R_{IN1}$  and  $R_{IN2}$ ) for the output tubes with the dual pot. In one suggestion, the wipers of the pots are tied to the power tube control grids. The contact integrity of the control wiper on the resistive element is not guaranteed, and any intermittent contact interrupts the bias feed to the output tubes. When this voltage disappears, the tube is inclined to draw as much current as possible, which will damage both the tube and the output transformer.

To avoid this situation, we may install the safety resistors  $R_s$  from the bias supply end of the pot to the wiper. If the wiper intermits,  $R_s$  should feed  $V-$  directly to the output tube. This should result in a current reduction and protect the transformer. Another solution is to wire the pot backwards, so that the resistive element replaces  $R_{IN1}$  and  $R_{IN2}$ . The wipers are connected to  $C_1$  and  $C_2$ .

Any DC current flow through a potentiometer will introduce DC noise. Pots become scratchy with normal use, and this is exacerbated by the presence of DC. We also run into potential low-frequency roll-offs with the reverse-wired connection, despite its slightly safer operation. Neither method is ideal, since they involve tampering with the critical bias

components. In this regard, we must strongly advise against this type of installation.

The two other types of power amp master volume involve altering the operating parameters of the power amp input stage. One of these methods works very well, while the second is not so successful. Both are explained in detail in the Power Amps chapter.

### **DISTORTION GENERATING TECHNIQUES**

There are three techniques used to generate distortion in guitar preamps, involving, respectively: 1) the optimization of bias levels of individual gain stages for specific harmonic enhancement; 2) cascaded gain stages to achieve cumulative distortion artifacts; and 3) signal bounding techniques to change the shape of the signal dramatically in one step. We will examine each in turn.

#### 1) Gain Stage Optimization

We know from the preceding chapters that we can vary the parameters of the individual gain stages widely. By altering  $R_K$ , we change the plate current and  $\mu$  point.

In Table 4-1, we saw that the signal output capability varies with  $I_K$  and  $R_A$ . The value of  $I_K$  has the ultimate control over the dynamic range of the stage. If  $I_K$  is 1mA, and  $V_p$  at idle is  $V+/2$ , then the peak signal output is  $V+/2$ . If  $R_A$  is held constant but  $I_K$  is reduced by increasing  $R_K$ , then  $V_A$  at idle will rise. Suppose  $V_A$  now equals  $3V+/4$ . The dynamic range for clean signals is restricted to  $V+/4$  as a peak value. However, although the positive signal excursion is limited to  $V+/4$ , the negative excursion is three times as large, at  $3V+/4$ .

To alter  $I_K$ , we changed the cathode resistor