

Figure 15. Modulator circuit, including a 12AU7 and two copper oxide varistors.²¹

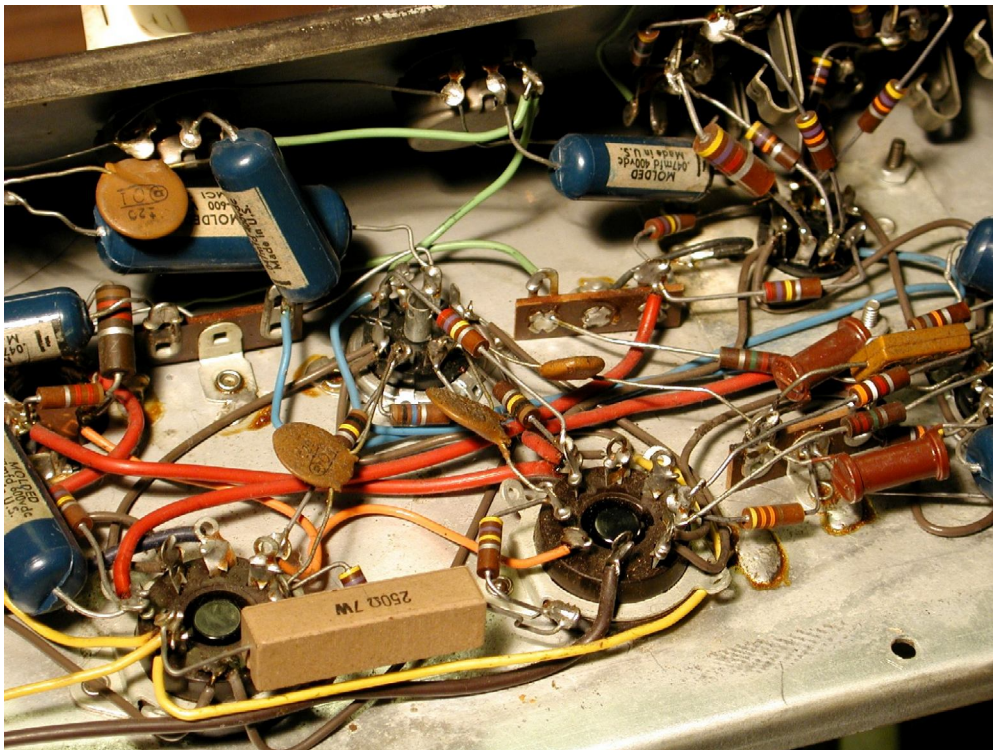


Figure 16. Photo includes the modulator circuit. Notice the two dumbbell-shaped varistors on the lower right.

²¹ Jourard