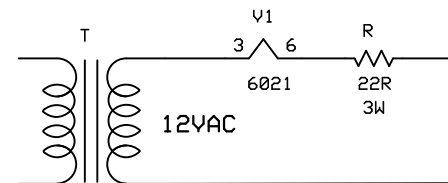



NO!

the 6V tube has 12V applied to the filament. not good.  
 - use a series R to balance or use two 6V .3A tubes in series.



YES!

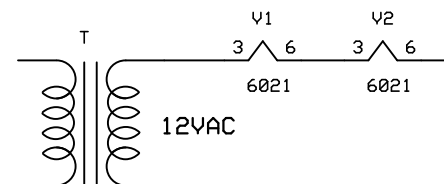single tube has series load resistor dropping 6V for tube,



YES!

the two tubes act as a voltage divider 6V / tube,

Company Name		
Schematic Name		
Designer's name	Rev 1.0	Page # or name
	11/11/2014	