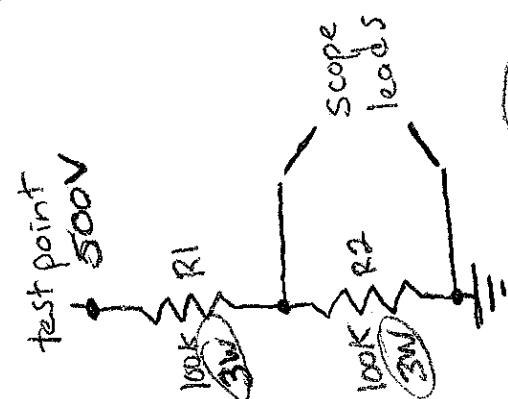


# Oscilloscope Voltage Reducer



$$V_{R2} = V_{RT} - V_{R1}$$

$$V_{R2} = 500 - 250$$

$$V_{R2} = 250V$$

$$P_{Tot} = 1.25W$$

$$I_T = \frac{V}{R_1 + R_2}$$

$$= \frac{500}{200,000}$$

$$= 0.0025A \text{ (2.5mA) ok loading?}$$

$$V_{R1} = I_{R1} \times R_1$$

$$= 0.0025 \times 100,000$$

$$= 250V$$

chassis ground

$$V_{R2} = V_{RT} - V_{R1}$$

$$V_{R2} = 500 - 250$$

$$V_{R2} = 250V$$

$$P_{Tot} = 1.25mW$$

$$I_T = \frac{V}{R_1 + R_2}$$



$$= \frac{500}{2,000,000}$$

$$= 0.00025 \text{ (250}\mu A) \text{ better loading?}$$


$$V_{R1} = I_{R1} \times R_1$$

$$= 0.00025 \times 1,000,000$$

$$= 250V$$

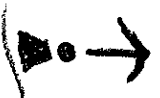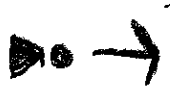

# Oscilloscope Voltage Reducer

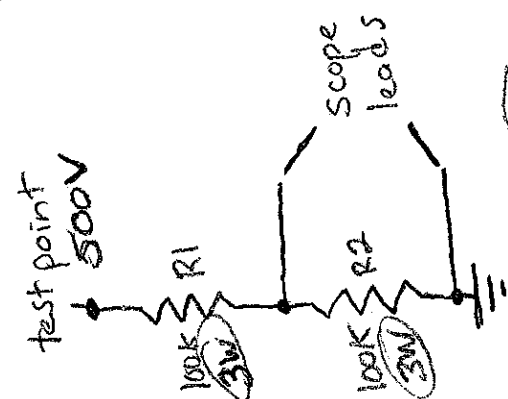

$$V_{R2} = V_{RT} - V_{R1}$$

$$V_{R2} = 500 - 250$$

$$V_{R2} = 250V$$

$$P_{Tot} = 1.25W$$

$$I_T = \frac{V}{R_1 + R_2}$$

$$= \frac{500}{200,000}$$

$$= 0.0025A \text{ (2.5mA) ok loading?}$$

$$V_{R1} = I_{R1} \times R_1$$

$$= 0.0025 \times 100,000$$

$$= 250V$$

chassis ground

$$V_{R2} = V_{RT} - V_{R1}$$

$$V_{R2} \approx 500 - 250$$

$$V_{R2} = 250V$$

$$P_{Tot} = 1.25mW$$

$$I_T = \frac{V}{R_1 + R_2}$$

$$= \frac{500}{2,000,000}$$

$$= 0.00025 \text{ (250uA) better loading?}$$

$$V_{R1} = I_{R1} \times R_1$$

$$= 0.00025 \times 1,000,000$$

$$= 250V$$

