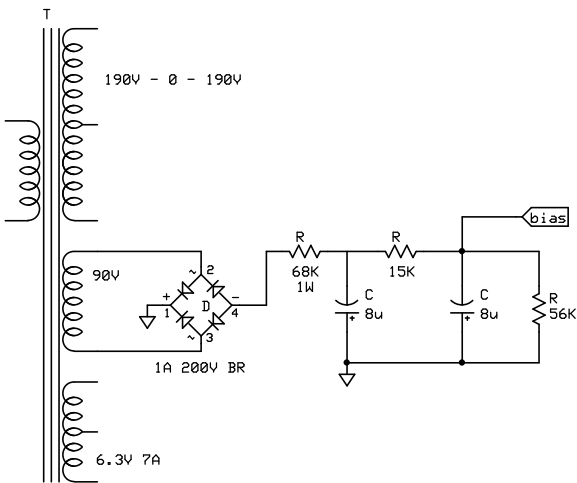
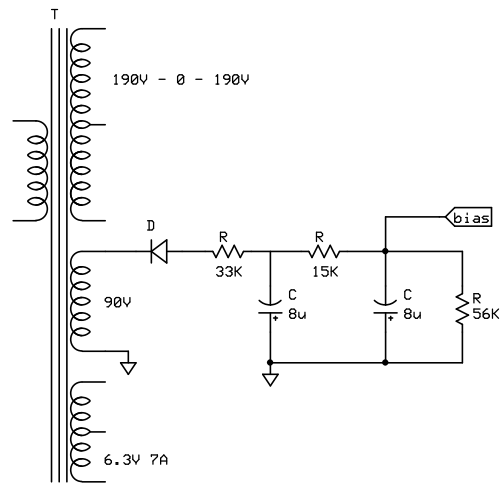




Using a FWB



Using a Half Wave

Either circuit will develop about -34V at the bias tap.

Forum Amps		
Marshall 90V Sec. Bias Supplies		
P. Mitcheltree	Rev 1.0	Page 1 of 1
	4/15/2018	